



## EEE111 Project

# Regulated DC power supply converts AC line voltage to a constant DC voltage for 4.3V

Asif Rahman	ID # 1821214042
Mossran Tahmid Khan	ID # 1821117042
Shahriar Hasan Shanto	ID # 2011465642
Saniyat Tamjit Niloy	ID # 2111801643

## Objective:

Regulated DC power supply converts AC line voltage to a constant DC voltage of 4.3.

## Introduction:

A regulated power supply (also known usually as a linear power supply) ensures that the output current remains constant, even if the input changes, by converting unregulated AC (alternating current) to a constant DC (direct current).

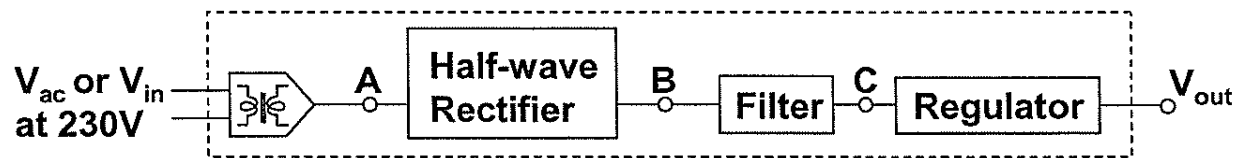


Fig1: Regulated DC Power Supply Diagram

## Equipment List:

Serial No	Component Details	Specification	Quantity
1	P-N Junction Diode	1N4007	4
2	Resistor	220Ω, 1KΩ	1
3	Stepdown Transformer	Input-220v 50hz Output-12v	1
4	Capacitor	220Uf	1
5	Zener Diode	1N4731A	1
6	Chords and wire		as required
7	Bread Board		1

Circuit Diagram:

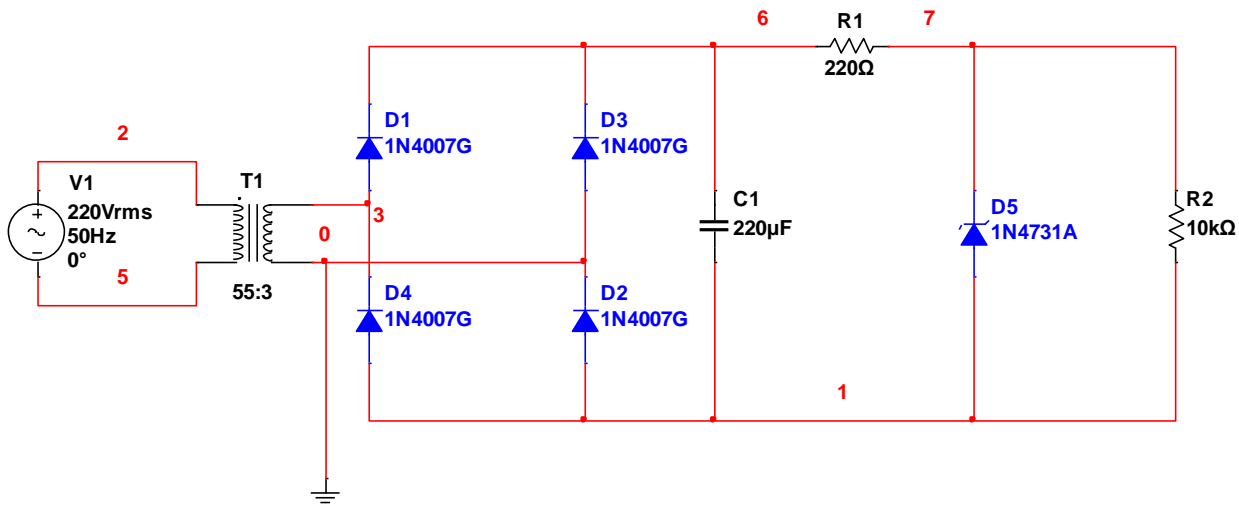


Fig2: Regulated DC power supply multisim diagram

Result (Simulation Result):

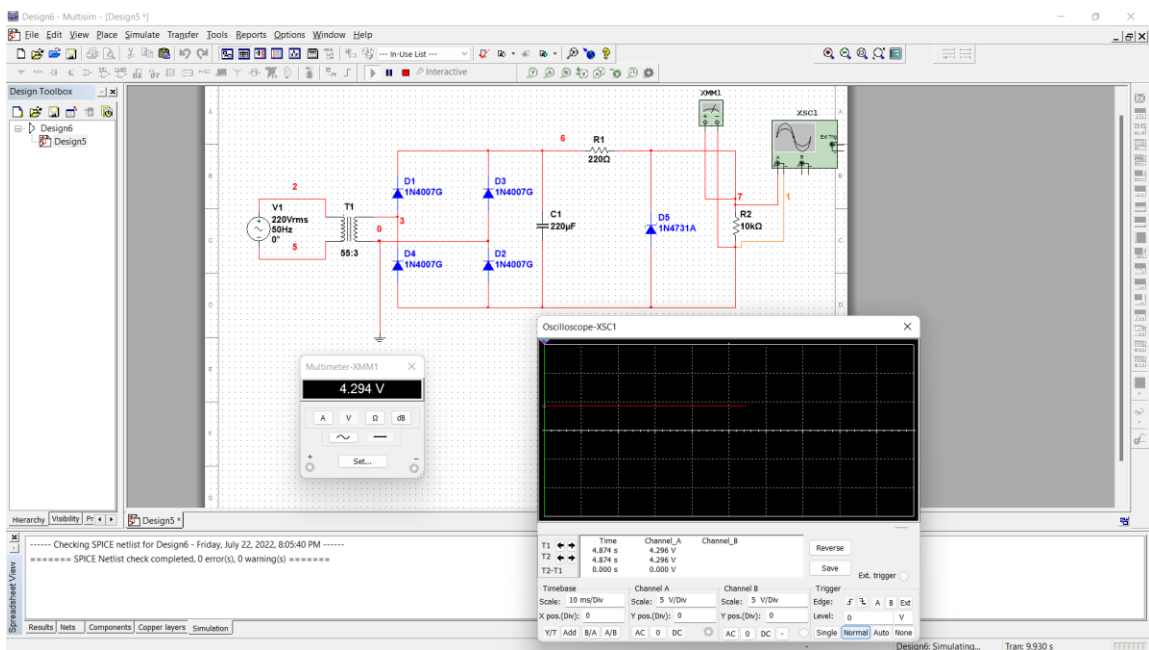


Fig3: Simulation result

## Mathematical Calculation:

$$V_2(PK) = (N_2/N_1) * V_1$$

$$= (3/55) * 220$$

$$= 12V$$

$$V_2(PK) = 12 * \sqrt{2}$$

$$= 16.97V$$

$$V(R_1) = 16.97 - 1.4$$

$$= 15.57V$$

$$I(R_1) = 15.57/220 = 70.77mA$$

$$T = 1/2f = 1/100 = 0.01$$

$$V_r = (I * t) / C = (70.77 * 0.01) / 220 = 3.21mV$$

$$V(R_1) > V_{zd} = 15.57 > 4.3 ; \text{ so, Zenner will Work.}$$

$$\text{Assume, } V_{zd} = V(R_2) = 4.3.$$

$$V(R_2) = I_2 * R_2$$

$$\Rightarrow 4.3 = I_2 * 10Kohm$$

$$\Rightarrow I_2 = 4.3 / (10Kohm)$$

$$\Rightarrow I_2 = 0.43mA$$

$$\text{So, } I_2 = 0.43mA$$

$$I_z = I(R_1) - I_2 = 70.77mA - 0.43mA = 70.34 mA$$

$$\text{So, } I_{zm} = 217mA \text{ \& } I_{zk} = 58 mA; I_{zk} < I_z < I_{zm}.$$

$$V(R_2) = 0.43mA * 10Kohm = 4.3 V.$$